Template Week 2 – Logic

Student number:

Assignment 2.1: Parking lot

Which gates do you need?

OR gate

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Assignment 2.2: Android/iPhone

Which gates do you need?

OR gate

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
0	1	1
1	0	1
1	1	1

Assignment 2.3: Four NAND gates

Complete this table


A	В	Q
0	0	1
0	1	1
1	0	1
1	1	0

How can the design be simplified?

The design can be simplified by using fewer NAND gates. For example, to make an AND gate, you can use two NAND gates: one to combine the inputs and another to reverse the result. This way, you don't use extra gates and keep it simple.


Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:

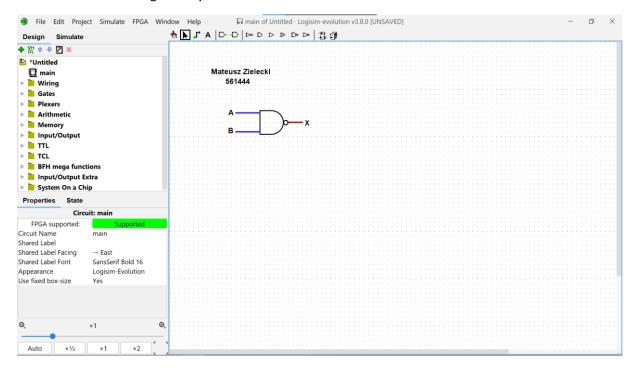

Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:

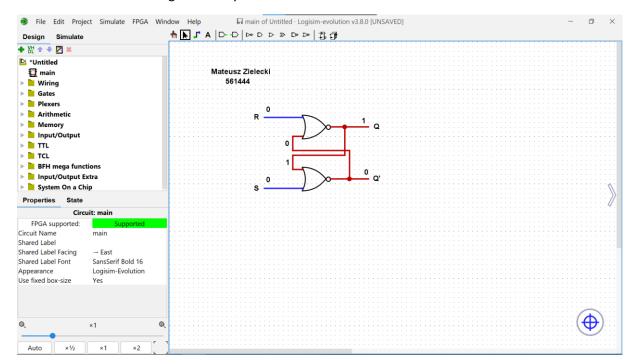

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

Bonus point assignment – week 2

Create a java program that accepts user input and presents a menu with options.


- 1. Is number odd?
- 2. Is number a power of 2?
- 3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Paste source code here, with a screenshot of a working application.

```
import java.util.Scanner;
public class Main {
  public static void main(String[] args) {
    Scanner scanner = new Scanner(System.in);
    System.out.println("Enter a number:");
    int number = scanner.nextInt();
    while (true) {
      System.out.println("\nMenu:");
      System.out.println("1. Check if the number is odd");
      System.out.println("2. Check if the number is a power of 2");
      System.out.println("3. Find the Two's complement of the number");
      System.out.println("4. Exit");
      System.out.print("Choose an option: ");
      int choice = scanner.nextInt();
      switch (choice) {
         case 1:
           System.out.println(isOdd(number));
           break;
         case 2:
           System.out.println(isPowerOfTwo(number));
           break;
         case 3:
           System.out.println(twosComplement(number));
           break;
         case 4:
           scanner.close();
           return;
         default:
           System.out.println("Something went wrong. Please try again.");
    }
  }
  public static boolean isOdd(int num) {
    return (num & 1) == 1;
  }
  public static boolean isPowerOfTwo(int num) {
    return num > 0 \&\& (num \& (num - 1)) == 0;
  public static int twosComplement(int num) {
    return ~num + 1;
}
```

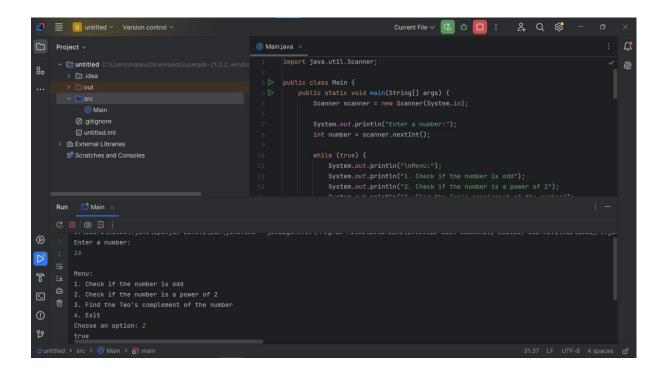

Ready? Then save this file and export it as a pdf file with the name: week2.pdf